

Homework & Solution for chapter 1

DIC


Instructor: Yuzhuo Fu

TA: Pengzhi Chu

Key points

- ▶ Moore law->predict trend
- ▶ Function description->Transistor-level schematic
- ▶ Transistor-level schematic <->Stick diagram
 - ▶ Area estimation for stick diagram

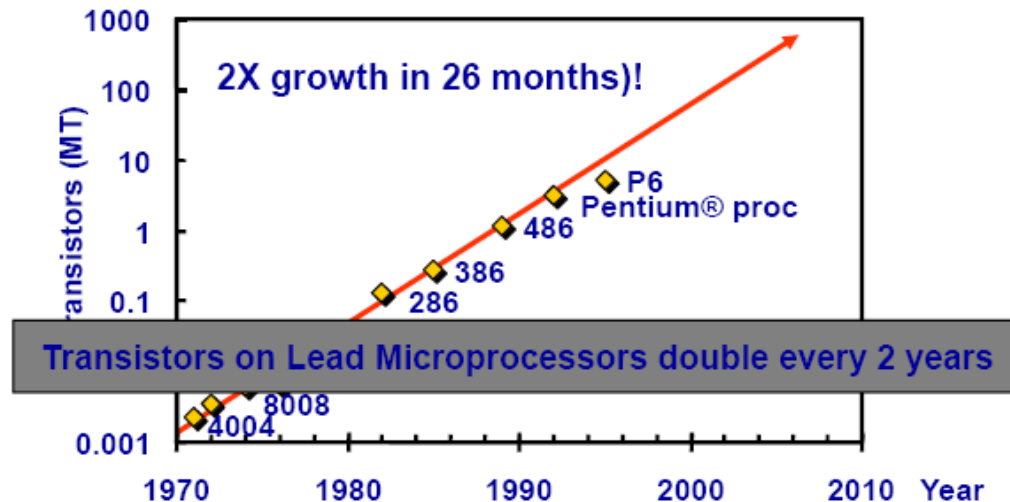- ▶ I - Extrapolating the data from figure, predict the transistor count of a microprocessor in 2010




Starting with 42,000,000 transistors in 2000 and doubling every 26 months for 10


years gives $42\text{M} \cdot 2^{\left(\frac{10 \cdot 12}{26}\right)} \approx 1\text{B}$ transistors.

NMOS:OR-> parallel; AND-> serial

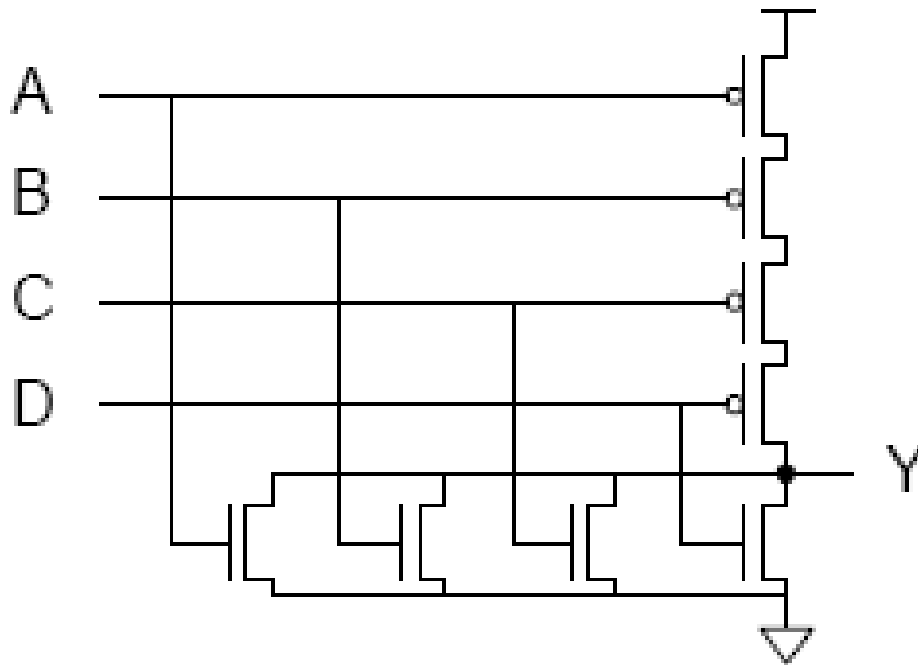- ▶ I-2 sketch a transistor-level schematic for a CMOS 4-input NOR gate



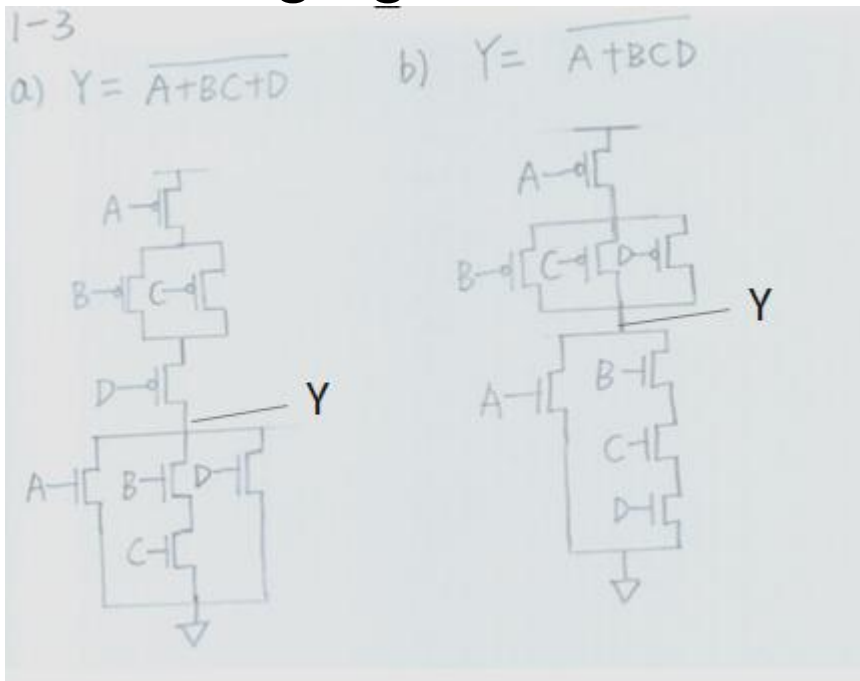
- ▶ 1-3 sketch a transistor-level schematic for a single-stage CMOS logic gate for each of the following functions:




$$\text{a) } Y = \overline{A+BC+D}$$

$$\text{b) } Y = \overline{A+BCD}$$

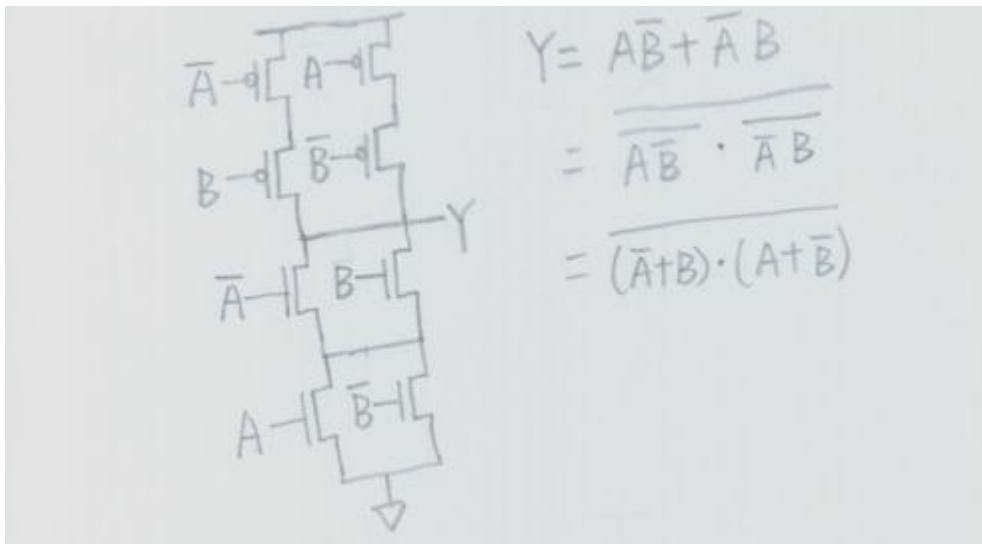-
- ▶ I-4 sketch a transistor-level schematic of a CMOS 2-input XOR gate. You may assume you have both true and complementary versions of the inputs available



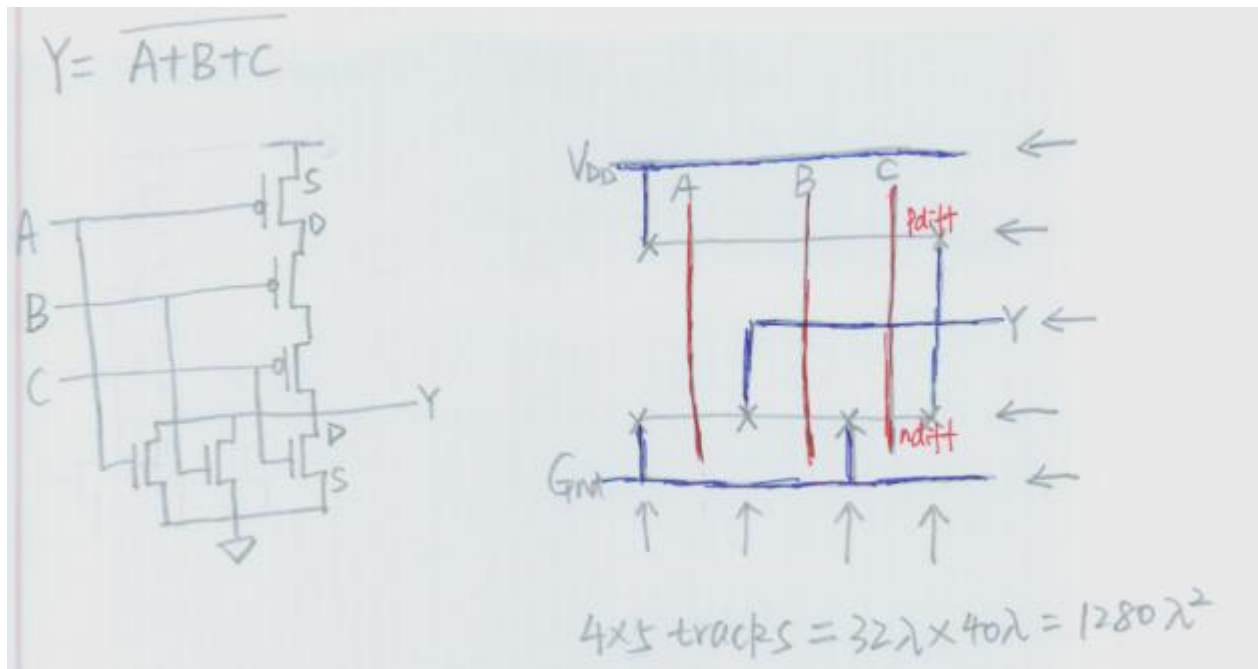- ▶ I-5 Sketch a stick diagram for a CMOS 3-input NOR gate
- ▶ I-6 estimate the area of I-5



- 1-7 sketch transistor-level schematic of the following logic functions. You may assume you have both true and complementary versions of the inputs available
 - a) 2:4 decoder defined by



$$Y0 = \overline{A0} \cdot \overline{A1}, Y1 = A0 \cdot \overline{A1}$$

$$Y2 = \overline{A0} \cdot A1, Y3 = A0 \cdot A1$$

  - b) 3:2 priority encoder defined by

$$Y0 = \overline{A0} \cdot (A1 + \overline{A2})$$

$$Y1 = \overline{A0} \cdot \overline{A1}$$







- 1-8 Use a combination of CMOS gates (represented by their symbols) to generate the following functions from A, B, and C

a) $Y = A$ (buffer)



b) $Y = A\bar{B} + \bar{A}B$ (XOR)

c) $Y = AB + \bar{A}\bar{B}$ (XNOR)



d) $Y = AB + BC + AC$ (SUM)

    

  - 1-9 sketch a side view(cross section) of the gate from X to X'




  - 1-10 translate the layout to circuit structure; estimate the area of the latch




► $4 \times 6 \text{ tracks} = (32+5+2) \text{ I} \times (48+2) \text{ I} = 1950 \text{ I}^2$

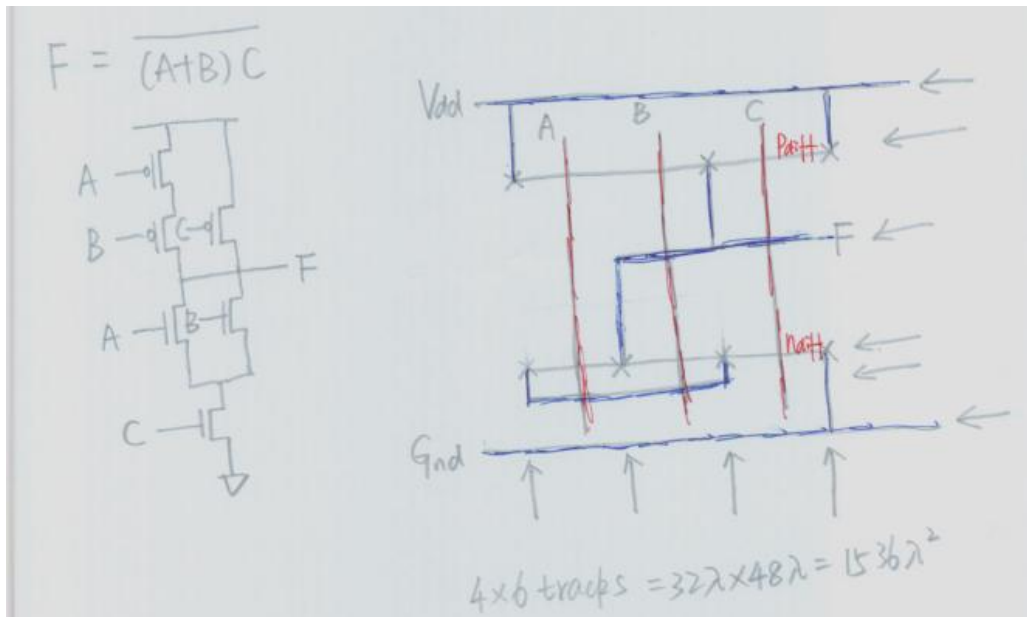- 1-10 consider the design of a CMOS compound OR-AND-INVERT(OA21)gate computing $F = \overline{(A+B)}C$
 - Sketch a transistor-level schematic
 - Sketch a stick diagram
 - Estimate the area from the stick diagram



 - 1-11 consider the design of a CMOS compound OR-AND-INVERT(OA22)gate computing $F = \overline{(A+B)(C+D)}$
 - Sketch a transistor-level schematic
 - Sketch a stick diagram
 - Estimate the area from the stick diagram



(c) 5×6 tracks = $40 \lambda \times 48 \lambda = 1920 \lambda^2$. (with a bit of care)

5×7 tracks = $40 \lambda \times 56 \lambda = 2240 \lambda^2$